



Worst case delay for e1:

z01 worst delay = 5
to0 worst delay = 7



inverter

z01: we start from $a0=1, b0=1, e0=1$ → in the way of $b0$ we have an inverter → inverter has 7ns delay for to0, then we have a nmos → nmos has 5ns for to2 → $7+5 = 12$
 so far we have 12ns delay and we're in j1.
 $a0, b0, e0$ started together so in 12ns delay of j1, $e0$ has done its job in 7ns, so $e0$ delay is not important. when j1 comes with 1, pmos should be 2 → pmos has 7ns for to2 → $12+7 = 19$
 then at last we have inverter and its to1 → $19+5 = \boxed{24}$

to0: we start from $a0=0, b0=1, e0=0$ → like the last one we have inverter and nmos in front of $b0$ → 12ns, and $e0$ did its job, so we are in j1 with the value of 0, and have a pmos that should go to1 or a nmos that should go to2, both of them are 5ns
 $12+5 = 17$, and we have an inverter that should go to0,

$$17+7 = \boxed{24}$$

worst case delay for $g1$:

to1: we start with $a0=0, b0=1, c0=1, g0=1$, we have inverter in front of $a0$ (we should go down from $a0$), so it has 5ns delay, but $c0$ in this 5ns has connected the nmos gate (it wants 4ns) and then $b0$ connects another nmos and then we have $4+4=8ns$, so the inverter of $a0$ is not counted in delay, we have another nmos so $\rightarrow 8+4=12$ and we have inverter to go to $K1$ $\rightarrow 12+5=17$, in this time $g0$ done its job and so we have to2 for pmos (7ns) or to0 for nmos (4ns) in front of $K1$. $\rightarrow 17+7=24$ and then another inverter $\rightarrow 24+5=29$

to0: we start from $a0=1, b0=0, c0=0, g0=0$, like last one we don't need $a0$'s inverter delay so we have three nmos that should go to2 $\rightarrow 3 \times 5=15ns$ and one inverter to0 $\rightarrow 15+7=22$ and $g0$ done its job in this time and we have to1 for pmos (5ns) or to2 for nmos (5ns) in front of $K1$ $\rightarrow 22+5=27$ and at last we have inverter to0 $\rightarrow 27+7=34$

Summary: $e1 \rightarrow \underline{to1} = 24$
 $\rightarrow \underline{to0} = 24$
 \Rightarrow BCS circuit worst case delay $\rightarrow \underline{to1} = 29$
 $\rightarrow \underline{to0} = 34$

$g1 \rightarrow \underline{to1} = 29$
 $\rightarrow \underline{to0} = 34$